


(Figure and table from: [http://www.interfacebus.com/Speed-Power\\_Chart.html](http://www.interfacebus.com/Speed-Power_Chart.html), visited 15APR04)

Device Families:

- TTL (74xx) True TTL
- 74L Low power
- 74S Schottky
- 74H High speed
- 74LS Low power - Schottky
- 74AS Advanced - Schottky
- 74ALS Advanced - Low power - Schottky
- 74F(AST) Fast - (Advanced - Schottky)
- 74C CMOS.....check Vcc levels
- 74HC (U) High speed - CMOS (Unbuffered output)
- 74HCT High speed - CMOS - TTL inputs
- 74AHC Advanced - High speed - CMOS
- 74AHCT Advanced - High speed - CMOS - TTL inputs
- 74FCT (-A) Fast - CMOS - TTL inputs (speed variations)
- 74FCT (-T, -AT) Fast - CMOS - TTL inputs (speed variations)
- 74AC Advanced - CMOS
- 74ACT Advanced - CMOS - TTL inputs
- 74FACT AC, ACT (Q) series
- 74ACQ Advanced - CMOS - Quiet outputs
- 74ACTQ Advanced - CMOS - TTL inputs - Quiet outputs

## TTL Inverter (Totem Pole Output)


*Practical inverter (NOT) circuit*

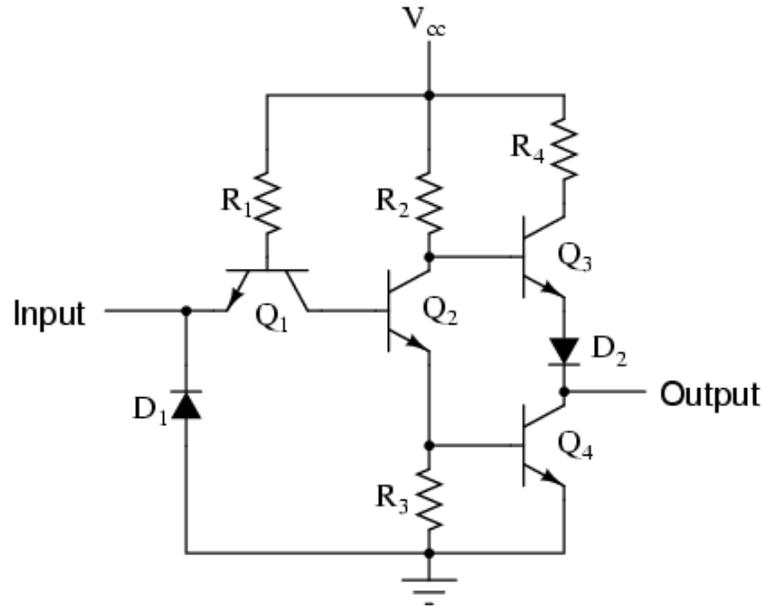

(source: <http://sub.allaboutcircuits.com/images/04073.png>)
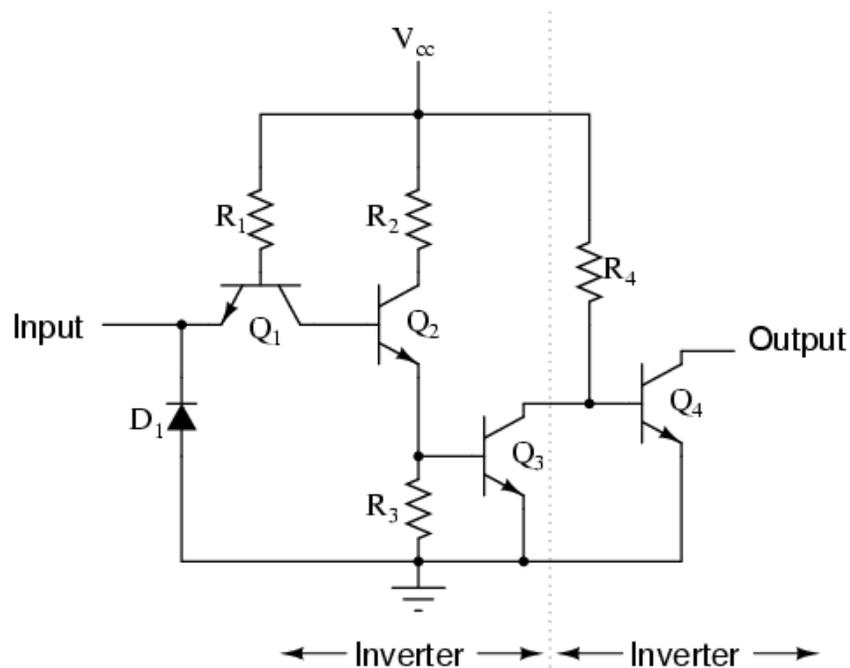
## TTL Buffer (Open-Collector Output)


*Buffer circuit with open-collector output*




(source: <http://sub.allaboutcircuits.com/images/04089.png>)

# CMOS Inverter

*Inverter circuit using IGFETs*

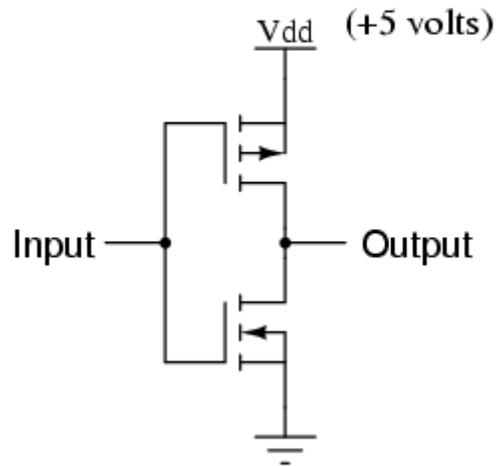

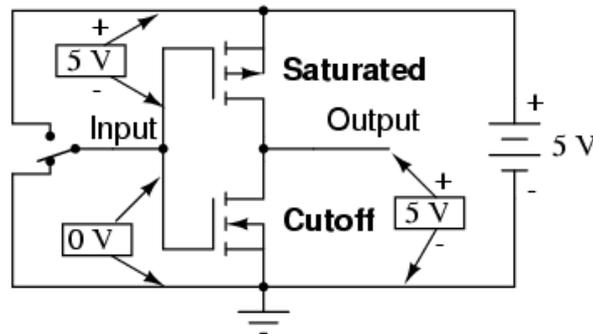
(source: <http://sub.allaboutcircuits.com/images/04132.png>)



Input = "low" (0)

Output = "high" (1)

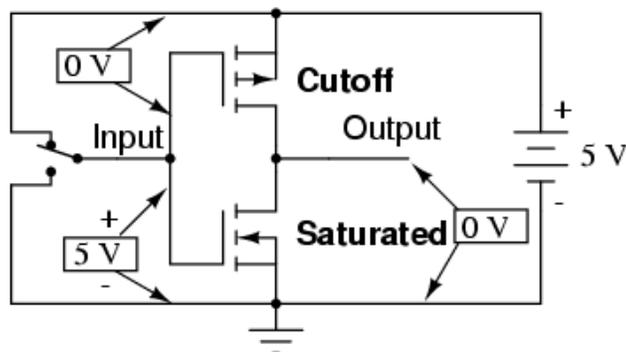(source: <http://sub.allaboutcircuits.com/images/04133.png>)



Input = "high" (1)

Output = "low" (0)

(source: <http://sub.allaboutcircuits.com/images/04134.png>)