
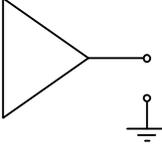
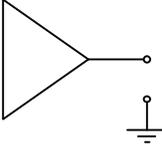
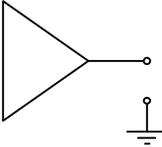
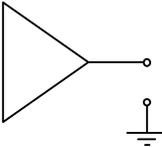
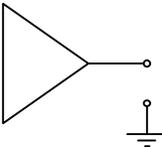


Op-amps


<p>Inverting Amplifier</p> 	<p>$V_o =$</p> <hr/> <p>$R_{in} =$ _____</p>
<p>Non-Inverting Amplifier</p> 	<p>$V_o =$</p> <hr/> <p>$R_{in} =$ _____</p>
<p>Summing Amplifier</p> 	<p>$V_o =$</p> <hr/> <p>$R_{in} =$ _____ for V_1 $R_{in} =$ _____ for V_2</p>
<p>Voltage Follower</p> 	<p>$V_o =$ _____</p> <hr/> <p>$R_{in} =$ _____</p>
<p>Differential Amplifier</p> 	<p>$V_o =$</p> <hr/> <p>$R_{in} =$ _____ for V_2 $R_{in} =$ _____ for V_1</p>

Limitations of Practical Operational Amplifiers

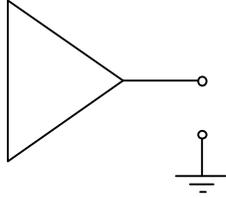
1. The output voltage of signal-type op-amps is limited to about 1 to 2 V below the supply voltage (which is typically ± 15 V). It will depend on the output current beyond about 10 mA.



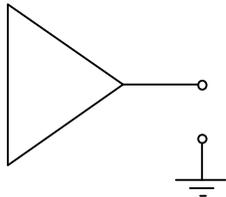2. The output current of signal-type op-amps is limited to about 10-20 mA.
(However, Power Op-Amps can handle much larger voltages and output currents.)



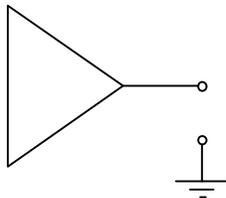3. The gain setting resistors should be kept within a range of about 1 k to 1 M to prevent noise, drift, and excessive circuit loading.



4. The gain of a typical op-amp should be limited to about 100 or less to prevent offset and drift

